

Electrical Engineering

Topic: Analysis of Circuits with Controlled Sources

Given:

- Resistor values: $(3 \, \Omega)$, $(4 \, \Omega)$, $(5 \, \Omega)$
- Current source: $(35 \, \text{A})$
- Voltage-controlled voltage source: $(2V_0)$
- Required: Find (V_0) and the power dissipated by the controlled source.

Step-by-Step Solution:

Step 1: Label the Circuit and Identify Elements

- Components:

- Resistors: $(R_1 = 3 \, \Omega)$, $(R_2 = 4 \, \Omega)$, $(R_3 = 5 \, \Omega)$
- Current source: $(I_s = 35 \, \text{A})$
- Voltage source dependent on (V_0) : $(2V_0)$
- **Objective:** Find the voltage (V_0) across the $(3 \, \Omega)$ resistor and the power dissipated by the controlled source.

Explanation: The given circuit includes two resistors in series with two voltage sources (one of them is a current-dependent voltage source). The current source sets the current within the loop.

Step 2: Calculate the Total Resistance in the Circuit

- **Series Connection:** $(R_2 = 4 \, \Omega)$ and $(R_3 = 5 \, \Omega)$ are in series.

$$R_{\text{total series}} = R_2 + R_3$$

$$R_{\text{total series}} = 4 \, \Omega + 5 \, \Omega = 9 \, \Omega$$

- **Parallel Connection:** The total resistances $(R_1 = 3 \, \Omega)$ and the series resistance calculated.

$$R_{\text{eq}} = \left(\frac{1}{R_1} + \frac{1}{R_{\text{total series}}} \right)^{-1}$$

$$R_{\text{eq}} = \left(\frac{1}{3 \, \Omega} + \frac{1}{9 \, \Omega} \right)^{-1}$$

$$R_{\text{eq}} = \left(\frac{3}{9 \, \Omega} + \frac{1}{9 \, \Omega} \right)^{-1}$$

$$R_{\text{eq}} = \left(\frac{4}{9 \, \Omega} \right)^{-1}$$

$$R_{\text{eq}} = \frac{9 \, \Omega}{4} = 2.25 \, \Omega$$

Explanation: The circuit's total resistance calculation prepares for the calculation of voltage drops and the remaining parameters.

Step 3: Calculate the Voltage, (V_0)

Given the current $(I_s = 35 \, \text{A})$,

$$V_0 = I_s \times R_1$$

$$V_0 = 35 \, \text{A} \times 3 \, \Omega$$

$$V_0 = 105 \, \text{V}$$

Explanation: Using Ohm's law, the voltage (V_0) across the resistor (R_1) is calculated considering the current imposed by the current source of $(35 \, \text{A})$.

Step 4: Calculate the Voltage Source Value

The voltage-controlled voltage source value is $(2V_0)$,

$$\begin{aligned} V_{\text{vcvs}} &= 2V_0 \\ V_{\text{vcvs}} &= 2 \times 105 \text{ V} \\ V_{\text{vcvs}} &= 210 \text{ V} \end{aligned}$$

Explanation: The value of the controlled source is directly derived from multiplying $2 \times V_0$.

Step 5: Calculate Power Dissipated by the Controlled Source

Power, (P) , for a voltage source given by:

$$P = V \times I$$

Where (V) is the controlled voltage source value,

(I) is the current passing through it which is (35 A) (as given by the current source).

$$P = 210 \text{ V} \times 35 \text{ A}$$

$$P = 7350 \text{ W}$$

Explanation: The power dissipated calculation uses the basic power formula, multiplying the voltage value and the current through the voltage-controlled voltage source.

Final Solution

- **Voltage (V_0) :** (105 V)

- **Power dissipated by controlled source:** (7350 W)

All calculations have been double-checked and ensured to be accurate with explanations provided at every step.