

## Series and Parallel Combinations of Resistors and Capacitors

### Given

- Resistances:
  - $R_1 = 1 \, \Omega$
  - $R_2 = 2 \, \Omega$
  - $R_3 = 1 \, \Omega$
  - $R_4 = 2 \, \Omega$
  - $R_5 = 1 \, \Omega$
  - $R_6 = 2 \, \Omega$
- Capacitances:
  - $C_1 = 1 \, \text{F}$
  - $C_2 = 2 \, \text{F}$
  - $C_3 = 2 \, \text{F}$
  - $C_4 = 2 \, \text{F}$
  - $C_5 = 1 \, \text{F}$

### Finding Equivalent Resistance

#### Step 1: Combine $R_1$ , $R_2$ , and $R_3$ in Series

The combined resistance of resistors in series:

$$R_{\text{series}} = R_1 + R_2 + R_3$$

$$R_{\text{series}} = 1 \, \Omega + 2 \, \Omega + 1 \, \Omega = 4 \, \Omega$$

**Explanation:** When resistors are in series, their resistances add up.

#### Step 2: Combine $R_4$ and $R_5$ in Parallel

The combined resistance of resistors in parallel:

$$\frac{1}{R_{\text{parallel}}} = \frac{1}{R_4} + \frac{1}{R_5}$$

$$\frac{1}{R_{\text{parallel}}} = \frac{1}{2 \, \Omega} + \frac{1}{1 \, \Omega}$$

$$\frac{1}{R_{\text{parallel}}} = 0.5 + 1$$

$$\frac{1}{R_{\text{parallel}}} = 1.5$$

$$R_{\text{parallel}} = \frac{1}{1.5} = \frac{2}{3} \, \Omega$$

**Explanation:** When resistors are in parallel, the reciprocal of their combined resistance is equal to the sum of the reciprocals of their individual resistances.

#### Step 3: Combine the Result from Step 2 with $R_6$ in Series

The combined resistance of resistors in series:

$$R_{\text{total}} = R_{\text{parallel}} + R_6$$

$$R_{\text{total}} = \frac{2}{3} \, \Omega + 2 \, \Omega$$

$$R_{\text{total}} = \frac{2}{3} + 2 = \frac{2}{3} + \frac{6}{3} = \frac{8}{3} \, \Omega$$

$$R_{\text{total}} = 2.67 \, \Omega$$

**Explanation:** Adding resistances in series results in the sum of the resistances.

#### Step 4: Combine the Result from Step 1 and Step 3 in Parallel

$$\frac{1}{R_{\text{eq}}} = \frac{1}{R_{\text{series}}} + \frac{1}{R_{\text{total}}}$$

$$\frac{1}{R_{\text{eq}}} = \frac{1}{4 \, \Omega} + \frac{1}{2.67 \, \Omega}$$

$$\frac{1}{R_{\text{eq}}} = 0.25 + 0.375$$

$$\frac{1}{R_{\text{eq}}} = 0.625$$

$$R_{\text{eq}} = \frac{1}{0.625} = 1.6 \, \Omega$$

**Explanation:** The reciprocal of the total resistance of parallel resistors is the sum of the reciprocals of each resistor's resistance.

## Finding Equivalent Capacitance

### Step 1: Combine $C_1$ and $C_2$ in Series

The combined capacitance of capacitors in series:

$$\frac{1}{C_{\text{series}}} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$\frac{1}{C_{\text{series}}} = \frac{1}{1 \text{ } \mu\text{F}} + \frac{1}{2 \text{ } \mu\text{F}}$$

$$\frac{1}{C_{\text{series}}} = 1 + 0.5$$

$$\frac{1}{C_{\text{series}}} = 1.5$$

$$C_{\text{series}} = \frac{1}{1.5} = \frac{2}{3} \text{ } \mu\text{F}$$

**Explanation:** Adding the reciprocals of the capacitances when in series results in the reciprocal of the total capacitance.

### Step 2: Combine $C_{\text{series}}$ with $C_3$ , $C_4$ and $C_5$ in Parallel

The combined capacitance of capacitors in parallel:

$$C_{\text{parallel}} = C_{\text{series}} + C_3 + C_4 + C_5$$

$$C_{\text{parallel}} = \frac{2}{3} \text{ } \mu\text{F} + 2 \text{ } \mu\text{F} + 2 \text{ } \mu\text{F} + 1 \text{ } \mu\text{F}$$

$$C_{\text{parallel}} = \frac{2}{3} + 5$$

$$C_{\text{parallel}} = \frac{2}{3} + \frac{15}{3}$$

$$C_{\text{parallel}} = \frac{17}{3} \text{ } \mu\text{F}$$

$$C_{\text{parallel}} = 5.67 \text{ } \mu\text{F}$$

**Explanation:** When capacitors are in parallel, their capacitances add up directly.

## Final Solutions

**Equivalent Resistance:**  $R_{\text{eq}} = 1.6 \text{ } \Omega$

**Equivalent Capacitance:**  $C_{\text{eq}} = 5.67 \text{ } \mu\text{F}$

These values represent the overall resistance and capacitance of the given circuit.