

## Operational Amplifier Circuit Analysis

### Given Data:

```
\( i_1 = 9 \text{ mA} \) \
\ ( i_2 = 6 \text{ mA} \) \
\ ( R_1 = 8 \text{ ohms} \) \
\ ( R_2 = 2 \text{ ohms} \) \
\ ( R_3 = 9 \text{ ohms} \) \
\ ( R_4 = 5 \text{ ohms} \) \
\ ( R_5 = 3 \text{ ohms} \) \
```

### Determine the voltages at the non-inverting input ( $V_+$ ) and inverting input ( $V_-$ ) of the op-amp:

#### Step 1: Voltage at $(V_+)$ :

```
\( V_1 = i_1 \cdot R_1 \) \
\ ( V_1 = 9 \text{ mA} \times 8 \text{ ohms} = 72 \text{ mV} \) \
```

#### Step 2: Voltage at $(V_-)$ :

```
\( V_2 = i_2 \cdot R_3 \) \
\ ( V_2 = 6 \text{ mA} \times 9 \text{ ohms} = 54 \text{ mV} \) \
```

#### Supporting Statement:

An ideal op-amp has negligible input current and the voltage difference between its input terminals in a closed-loop configuration is zero. Thus,  $(V_+ = V_-)$ .

```
\( V_+ = 72 \text{ mV} \) \
\ ( V_- = 54 \text{ mV} \) \
```

**Note:** Due to the ideal op-amp assumption,  $(V_+)$  and  $(V_-)$  are same, i.e.,  $(V_+ = V_-)$ .

### Calculate the output voltage $(V_{out})$ using virtual short concept:

```
\( V_{out} = V_- \left(1 + \frac{R_5}{R_4}\right) \) \
\ ( V_{out} = 72 \text{ mV} \left(1 + \frac{3 \text{ ohms}}{5 \text{ ohms}}\right) \) \
```

#### Supporting Statement:

An ideal op-amp will amplify the difference between its inputs based on the circuit configuration, here as a non-inverting configuration having feedback.

### Solve the equation to find $(V_{out})$ :

```
\( V_{out} = 72 \text{ mV} \left(1 + 0.6\right) \) \
\ ( V_{out} = 72 \text{ mV} \times 1.6 \) \
\ ( V_{out} = 115.2 \text{ mV} \) \
```

**Determine  $i_{out}$ :**

$$i_{out} = \frac{V_{out}}{R_5}$$
$$i_{out} = \frac{115.2 \text{ mV}}{3 \text{ ohms}}$$
$$i_{out} = 38.4 \text{ mA}$$

### Final Solution:

The value of the output current  $i_{out}$  is  $38.4 \text{ mA}$ .

#### Supporting Statement:

The final output current is calculated using Ohm's Law by dividing the derived  $V_{out}$  by the respective resistance in the circuit.