

DC Circuit Analysis

Subject: Electrical Engineering

Topic: DC Circuit Analysis

Given and Introduction:

The circuit in question consists of a 12V DC source, a 1Ω resistor, a 5Ω resistor, an inductor of 2H, a 4Ω resistor, and a capacitor of 1F.

Solution Steps:

(a) To find the current (i_L) through the inductor:

1. Steady-State Current through Resistor Circuit (No Transient Components):

For a DC steady-state condition, the inductor will behave as a short circuit because the voltage across the inductor is zero in a steady state ($V_L = L \frac{di}{dt} = 0$)

2. Combining the Resistors:

At steady state, combine resistors to simplify the circuit:

- Combining 4Ω resistor in parallel with the short-circuited branch: Since the inductor acts like a short, the parallel combination of 4Ω and 0Ω results in 0Ω (effective resistance zero).

3. Effective Series Resistance:

Combine remaining resistances in series:

$$R_{\text{total}} = 1\Omega + 5\Omega = 6\Omega$$

4. Applying Ohm's Law:

Calculate the current from the source (I) through the effective resistor:

$$I = \frac{V}{R_{\text{total}}} = \frac{12V}{6\Omega} = 2A$$

Because of steady-state, the same current flows through the inductor since the inductor is treated as a short circuit in steady state.

Thus, the current (i_L) through the inductor is $(2A)$.

(b) To find the current (i) through the 1Ω resistor:

As determined from the previous step, the same current (I) flows through the 1Ω resistor in series.

Thus, the current (i) through the 1Ω resistor is also $(2A)$.

(c) To find the voltage (v_C) across the capacitor:

1. Applying Kirchhoff's Voltage Law:

At steady state, the voltage across the capacitor will be the same as across the 4Ω resistor since they are in parallel. Given that 4Ω is effectively bypassed by the short-circuited inductor.

2. Effective Voltage across Combined Resistor:

Calculate the potential difference across 5Ω resistor:

$$V_{5\Omega} = I \times 5\Omega = 2A \times 5\Omega = 10V$$

So, the remaining voltage drops across 1Ω resistor and battery terminations should add to 12V. Thus there is no drop across capacitor.

Thus, the voltage (v_C) across the capacitor is $(0V)$.

(d) To find the energy stored in the inductor:

1. Using the formula for energy stored in the inductor:

$$W_L = \frac{1}{2} L i_L^2$$

Where $(L = 2H)$ and $(i_L = 2A)$,

2. Substituting the values:

$$W_L = \frac{1}{2} \times 2H \times (2A)^2 = \frac{1}{2} \times 2 \times 4 = 4 \text{ J}$$

Thus, the energy stored in the inductor is $(4J)$.

(e) To find the energy stored in the capacitor:

1. Using the formula for the energy stored in the capacitor:

$$W_C = \frac{1}{2} C v_C^2$$

Where $C = 1\text{F}$ and $v_C = 0\text{V}$,

2. Substituting the values:

$$W_C = \frac{1}{2} \times 1\text{F} \times (0\text{V})^2 = 0\text{J}$$

Thus, the energy stored in the capacitor is 0J .

Final Solutions:

- (a) The current i_L through the inductor $= 2\text{A}$
- (b) The current i through the 1Ω resistor $= 2\text{A}$
- (c) The voltage v_C across the capacitor $= 0\text{V}$
- (d) The energy stored in the inductor $= 4\text{J}$
- (e) The energy stored in the capacitor $= 0\text{J}$